

Roll. No

200090102016

B. Tech. IV Semester Examination 2022

Branch: EC

Subject Code: TEC-242

M. M: 120

Subject Name: Analog Circuits

Time: 3 Hours

Q1. Answer the following questions (very short answers):

(5x2=10 Marks)

- For a silicon npn transistor, the base-to-emitter voltage (V_{BE}) is 0.7V and collector- to-base voltage is 0.2V, then write the region of operation of the transistor.
- A bipolar transistor is operating in the active region with collector current of 1mA. Assuming that the β of the transistor is 100 and the thermal voltage (V_T) is 25mV. What are the value of transconductance (g_m) and input resistance (r_π) of the transistor in the common –emitter configuration.
- For a voltage series feedback, what is the effect on input and output resistances with feedback when compared to without feedback?
- In an LC oscillator, if the value of L is increased five times then what will be the change in its frequency of oscillation?
- A high frequency amplifier has midband gain of 40 dB and higher cut-off frequency of 560 MHz. Find the gain of amplifier at 560 MHz frequency.

Q2. Answer the following questions (short answers):

(5x4=20 Marks)

- Why bootstrapping is required in emitter follower?
- How noise performance is affected with application of negative feedback in amplifiers?
- The circuit shown in fig.1 has an ideal op-amp. Find the oscillation frequency and condition to sustain the oscillations.

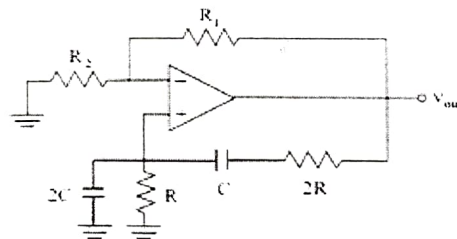



Fig.1

- Write the characteristics of Ideal Op-Amp.
- Explain the early effect in the NPN BJT with proper diagram?

Q3. All questions from UNIT-I. Parts (a) is compulsory and attempt any one part from part (b) or part (c).

- Find the overall voltage gain of the amplifier circuit given the Fig.2. Assume following parameters $h_{ie}=1.1k$, $h_{fe}=50$ and $V_A=\infty$.

6 Marks

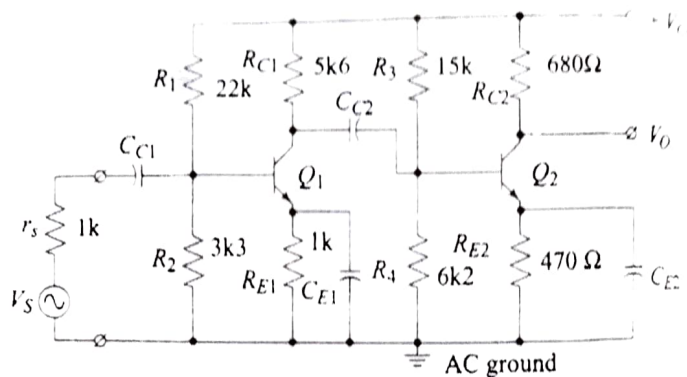

$$5k6 = 5.6k$$

$$3k3 = 3.3k$$

Fig.2

- (b) Derive the expression for voltage gain, input impedance and output impedance of Common emitter amplifier with degenerate resistance R_E . (12 Marks)
- (c) Derive the expression for voltage gain, input impedance and output impedance for the common base amplifier. (12 Marks)

Q4. All questions from UNIT-I. Parts (a) is compulsory and attempt any one part from part (b) or part (c).

- (a) Write the properties of negative feedback. (6 Marks)
- (b) Derive the expression for voltage gain, input impedance and output impedance of a current shunt feedback connection. (12 Marks)
- (c) Fig-3 depicts the bipolar feedback amplifier. Assuming R_1+R_2 is not very large, $\beta \gg \infty$ and $V_A = \infty$, Determine the closed-loop voltage gain, input impedance and output impedance. (12 Marks)

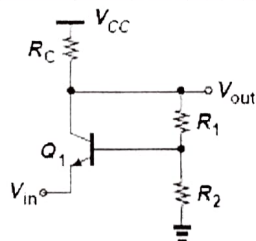


Fig.3

Q5. All questions from UNIT-I. Parts (a) is compulsory and attempt any one part from part (b) or part (c).

- (a) How oscillations are started in a sinusoidal oscillator? Give the necessary conditions for sinusoidal oscillations. (6 Marks)
- (b) Derive the expression for oscillation frequency of an RC phase shift oscillator using Op-amp. Further, find the condition to sustain the oscillations. (12 Marks)
- (c) With the help of a circuit diagram, explain the working of a monostable multivibrator. (12 Marks)

Q6. All questions from UNIT-IV. Parts (a) is compulsory and attempt any one part from part (b) or part (c).

- (a) A BJT has $h_{fe}=150$, $C_e=2\text{pF}$, $C_c=0.3\text{pF}$ and biased at $I_c=0.5\text{mA}$. Find the short circuit current gain cut-off frequency and unity current gain frequency of the transistor. **(6 Marks)**
- (b) Draw the small signal high frequency equivalent circuit of the common emitter amplifier circuit and find the voltage gain using inspections by poles of the given circuit in terms of g_m , R_L , R_S , C_μ , C_π and C_{CS} . **(12 Marks)**

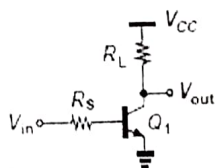


Fig-4

- (c) Derive the expression for cut-off frequency and unity gain bandwidth for the common emitter high frequency hybrid- π model **(12 Marks)**

Q7. All questions from UNIT-IV. Parts (a) is compulsory and attempt any one part from part (b) or part (c).

- (a) Define output offset voltage, input bias current, input offset current and common mode rejection ratio **(6 Marks)**
- (b) Explain the operation of a class A power amplifier and derive the expression for maximum power efficiency. **(12 Marks)**
- (c) Find the gain V_O / V_i for the given circuit **(12 Marks)**

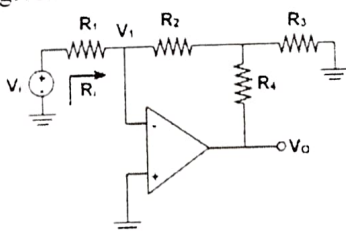


Fig.5.